

# CSU22022 Computer Architecture I

Prof. Michael Manzke

Processor Assignment: Full Project

## Instructions for the Blackboard Submission of the Assignment

20<sup>th</sup> November 2022

Version 1.0

The “Processor Assignment: Full Project” document (CSU22022 Processor Project 2022-2023 V1.0.pdf) specifies the VHDL entities that you need to implement.

It also provides names for all the entities (e.g., RF\_Register32Bit\_XXXXXXXX) with XXXXXXXX as your student ID and its instantiation names (e.g., RegisterXX, XX=00 to 31; TempRegXX, XX=01 to 15) with XX as the running number of the instantiation.

The file that implements the entity must have this name (e.g., RF\_Register32Bit\_XXXXXXXX.vhd) and the entity itself must have the same name (e.g., **entity** RF\_Register32Bit\_XXXXXXXX **is**).

Any instantiation of this entity must use the specified instantiation name (e.g., Register02: RF\_Register32Bit\_XXXXXXXX **port map**(...); ).

All files associated with this entity must also follow this naming convention: (e.g., RF\_Register32Bit\_XXXXXXXX.vhd

RF\_Register32Bit\_XXXXXXXX\_TB.vhd

RF\_Register32Bit\_XXXXXXXX\_SchematicXX.jpg

RF\_Register32Bit\_XXXXXXXX\_TDXX.jpg

RF\_Register32Bit\_XXXXXXXX\_Doc.pdf)

**Entities that do not comply with this naming convention will receive a zero mark.**

Furthermore, the “Processor Assignment: Full Project Checklist” document (CSU22022 Processor Project 2022-2023 Checklist V1.0.pdf) specifies the order in which you must implement, test, and document the entities, e.g.

01	RF_Mux16_32Bit_XXXXXXX.vhd	
	RF_Mux16_32Bit_XXXXXXX_TB.vhd	
	RF_Mux16_32Bit_XXXXXXX_SchematicXX.jpg	
	RF_Mux16_32Bit_XXXXXXX_TDXX.jpg	
	RF_Mux16_32Bit_XXXXXXX_Doc.pdf (only if needed)	
	Is working	

02	RF_Mux32_32Bit_XXXXXXX.vhd	
	RF_Mux32_32Bit_XXXXXXX_TB.vhd	
	RF_Mux32_32Bit_XXXXXXX_SchematicXX.jpg	
	RF_Mux32_32Bit_XXXXXXX_TDXX.jpg	
	RF_Mux32_32Bit_XXXXXXX_Doc.pdf (only if needed)	
	Is working	

Only fully implemented, tested, and documented entities should be ticked on the checklist and submitted to Blackboard. Before you make ticks for an entity, you must have all these documents: Entity\_XXXXXXX.vhd, Entity\_XXXXXXX\_TB.vhd, Entity\_XXXXXXX Entity\_SchematicXX.jpg, Entity\_XXXXXXX\_TDXX.jpg, and Entity\_XXXXXXX\_Doc.jpg (only if needed). Also, you must confirm that the entity is working.

**Partially implemented, tested, and documented entities (e.g., the timing diagrams are not annotated) will receive a zero mark.**

Partially implemented, tested, and documented entities should not be ticked on the checklist and no files for this entity should be submitted to Blackboard.

**Therefore, if you ticked on the checklist and submitted the entities 01 to 07 and it transpires that you didn't annotate the timing diagrams for entity 05, you will receive a mark for entities 01 to 04 but a zero mark for the entities 05 to 07.**

Please find following an example for a fully implemented, tested, and documented entities:

<b>XX</b>	RippleCarryAdder3Bit_XXXXXXX.vhd	☑
	RippleCarryAdder3Bit_XXXXXXX_TB.vhd	☑
	RippleCarryAdder3Bit_XXXXXXX_SchematicXX.jpg	☑
	RippleCarryAdder3Bit_XXXXXXX_TDXX.jpg	☑
	RippleCarryAdder3Bit_XXXXXXX_Doc.pdf (only if needed)	☑
	Is working	☑

## RippleCarryAdder3Bit XXXXXXXX.vhd

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity RippleCarryAdder3Bit_XXXXXXX is
```

```
    Port ( A : in STD_LOGIC_VECTOR (2 downto 0);
          B : in STD_LOGIC_VECTOR (2 downto 0);
          C_IN : in STD_LOGIC;
          SUM : out STD_LOGIC_VECTOR (2 downto 0);
          C_OUT : out STD_LOGIC;
          V : out STD_LOGIC);
```

```
end RippleCarryAdder3Bit_XXXXXXX;
```

```
architecture Behavioral of RippleCarryAdder3Bit_XXXXXXX is
```

```
    COMPONENT FullAdder_XXXXXXX
```

```
    PORT(
        A : in STD_LOGIC;
        B : in STD_LOGIC;
        C_IN : in STD_LOGIC;
        SUM : out STD_LOGIC;
        C_OUT : out STD_LOGIC
    );
    END COMPONENT;
```

```
    Signal C0_to_C1, C1_to_C2, C2_to_COut : STD_LOGIC;
```

```
begin
```

```
-- Instantiate Full Adder Bit 0
BIT0: FullAdder_XXXXXXX PORT MAP (
    A => A(0),
    B => B(0),
    C_IN => C_IN,
    SUM => SUM(0),
    C_OUT => C0_to_C1
);
```

```
-- Instantiate Full Adder Bit 1
BIT1: FullAdder_XXXXXXX PORT MAP (
```

```

    A => A(1),
    B => B(1),
    C_IN => C0_to_C1,
    SUM => SUM(1),
    C_OUT => C1_to_C2
);

-- Instantiate Full Adder Bit 2
BIT2: FullAdder_XXXXXXX PORT MAP (
    A => A(2),
    B => B(2),
    C_IN => C1_to_C2,
    SUM => SUM(2),
    C_OUT => C2_to_COut
);

-- Carry and Overflow
C_OUT <= C2_to_COut
V <= C2_to_COut XOR C1_to_C2 after 3ns;

end Behavioral;

```

**You may work with other students, but you cannot share code.  
Sharing code is plagiarism.**

### **RippleCarryAdder3Bit\_XXXXXXX\_TB.vhd**

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity RippleCarryAdder3Bit_XXXXXXX_TB is
-- Port ( ); We don't need ports
end RippleCarryAdder3Bit_XXXXXXX_TB;

architecture Sim of RippleCarryAdder3Bit_XXXXXXX_TB is

-- Component Declaration for the Unit Under Test (UUT)

component RippleCarryAdder3Bit_XXXXXXX
Port ( A : in STD_LOGIC_VECTOR (2 downto 0);
      B : in STD_LOGIC_VECTOR (2 downto 0);
      C_IN : in STD_LOGIC;
      SUM : out STD_LOGIC_VECTOR (2 downto 0);
      C_OUT : out STD_LOGIC;
      V : out STD_LOGIC);
end component;

--Inputs

signal A_TB : STD_LOGIC_VECTOR (2 downto 0) := (others => '0');
signal B_TB : STD_LOGIC_VECTOR (2 downto 0) := (others => '0');
signal C_IN_TB : STD_LOGIC := '0';

--Outputs

signal SUM_TB : STD_LOGIC_VECTOR (2 downto 0) := (others => '0');

```

```

signal C_OUT_TB : STD_LOGIC := '0';
signal V_TB : STD_LOGIC := '0';

begin

-- Instantiate the Unit Under Test (UUT)
uut: RippleCarryAdder3Bit_XXXXXXX PORT MAP (
    A => A_TB,
    B => B_TB,
    C_IN => C_IN_TB,
    SUM => SUM_TB,
    C_OUT => C_OUT_TB,
    V => V_TB
);

stim_proc: process
begin

-- Test Vector A

    A_TB <= "101";
    B_TB <= "110";
    C_IN_TB <= '0';

    wait for 60 ns;

-- Test Vector B

    A_TB <= "101";
    B_TB <= "111";
    C_IN_TB <= '0';

    wait for 60 ns;

-- Test Vector C

    A_TB <= "001";
    B_TB <= "011";
    C_IN_TB <= '0';

    wait for 60 ns;

-- Test Vector D

    A_TB <= "001";
    B_TB <= "010";
    C_IN_TB <= '0';

    wait for 60 ns;

-- Test Vector E

    A_TB <= "010";
    B_TB <= "110";
    C_IN_TB <= '0';

    wait for 60 ns;

```

-- Test Vector F, worst case propagation delay

```
A_TB <= "110";  
B_TB <= "001";  
C_IN_TB <= '1';
```

wait for 60 ns;

```
end process;  
end Sim;
```

**You may not use loops in your VHDL design or simulation code.**

### RippleCarryAdder3Bit XXXXXXXX Doc.pdf

A	Negative number + negative number with overflow flag (V-flag)									
	V <= C3 XOR C2									
	1									
	C3	C2	C1	C0	Unsigned value					
	1	0	0	0	Two's complement					
	A	A2	A1	A0	5	-3				
	B	B2	B1	B0	6	-2				
	+									
	SUM	S2	S1	S0	11	-5				
		1	0	1						

B

Negative number + negative number without overflow flag (V-flag)									
		V <= C3 XOR C2							
		0							
		C3	C2	C1	C0	Unsigned value			
		1	1	1	0	Two's complement			
A		A2	A1	A0		5	-3		
		1	0	1					
B		B2	B1	B0					
		1	1	1		7	-1		
+									
SUM		S2	S1	S0					
		1	1	0	0	12	-4		

C	Positive number + positive number with overflow flag (V-flag)							
	V <= C3 XOR C2							
	1							
	C3	C2	C1	C0	Unsigned value			
	0	1	1	0	Two's complement			
	A	A2	A1	A0	1	1		
		0	0	1				
	B	B2	B1	B0				
		0	1	1	3	3		
	+							
SUM	S2	S1	S0					
	0	1	0	0	4	-4		

D

Positive number + positive number without overflow flag (V-flag)							
V <= C3 XOR C2							
	C3	C2	C1	C0			
	0	0	0	0			
A	A2	A1	A0				
	0	0	1		1	1	
B	B2	B1	B0				
	0	1	0		2	2	
+							
SUM	S2	S1	S0				
	0	0	1	1	3	3	


E

Positive number + negative number without overflow flag (V-flag)							
V <= C3 XOR C2							
0							
	C3	C2	C1	C0	Unsigned value		
	1	1	0	0	Two's complement		
A		A2	A1	A0	2	2	
		0	1	0			
B		B2	B1	B0	6	-2	
		1	1	0			
+							
SUM		S2	S1	S0	8	0	
	1	0	0	0			

F	Negative number + positive number without overflow flag (V-flag)					
	Worst case propagation delay, C0 is set					
	V <= C3 XOR C2					
	0					
	C3	C2	C1	C0	Unsigned value	
	1	1	1	1	Two's complement	
	A	A2	A1	A0	6	-2
		1	1	0		
	B	B2	B1	B0		
		0	0	1	1	1
	+					
	SUM	S2	S1	S0		
	1	0	0	0	8	0
						C0 = 1 Important

Depending on the complexity of your testbench you may need a separate document (e.g., RippleCarryAdder3Bit\_XXXXXXX\_Doc.pdf) to specify the evaluation of your VHDL design. Otherwise, you can do this on the waveform screenshot, but the waveform screenshot must be in the JPG-file format.

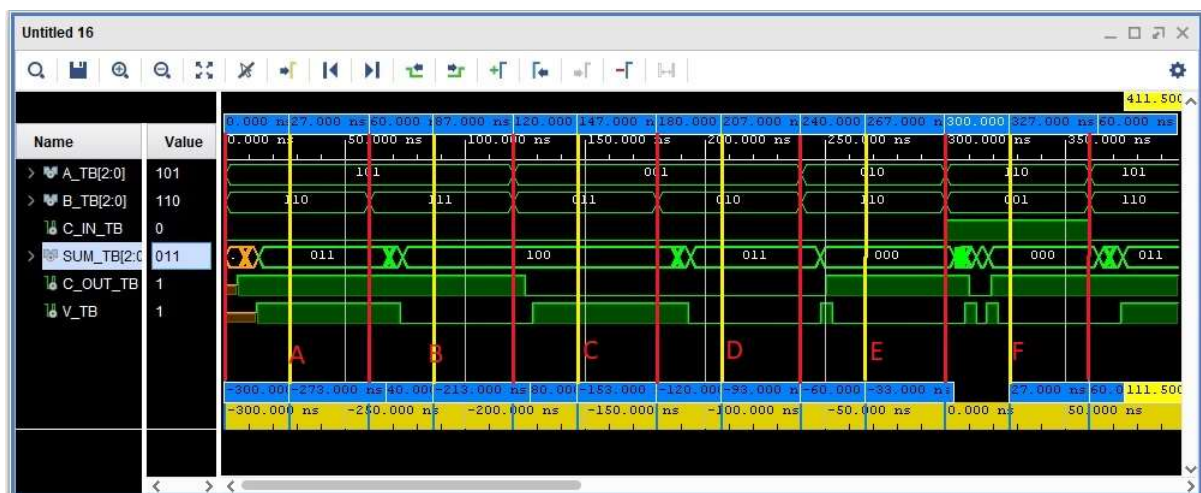
### RippleCarryAdder3Bit\_XXXXXXX\_TD01.jpg



You must take a screenshot of the waveform and save it in the JPG-file format. Important, you must annotate the waveform. In this case with reference to the RippleCarryAdder3Bit\_XXXXXXX\_Doc.pdf document.



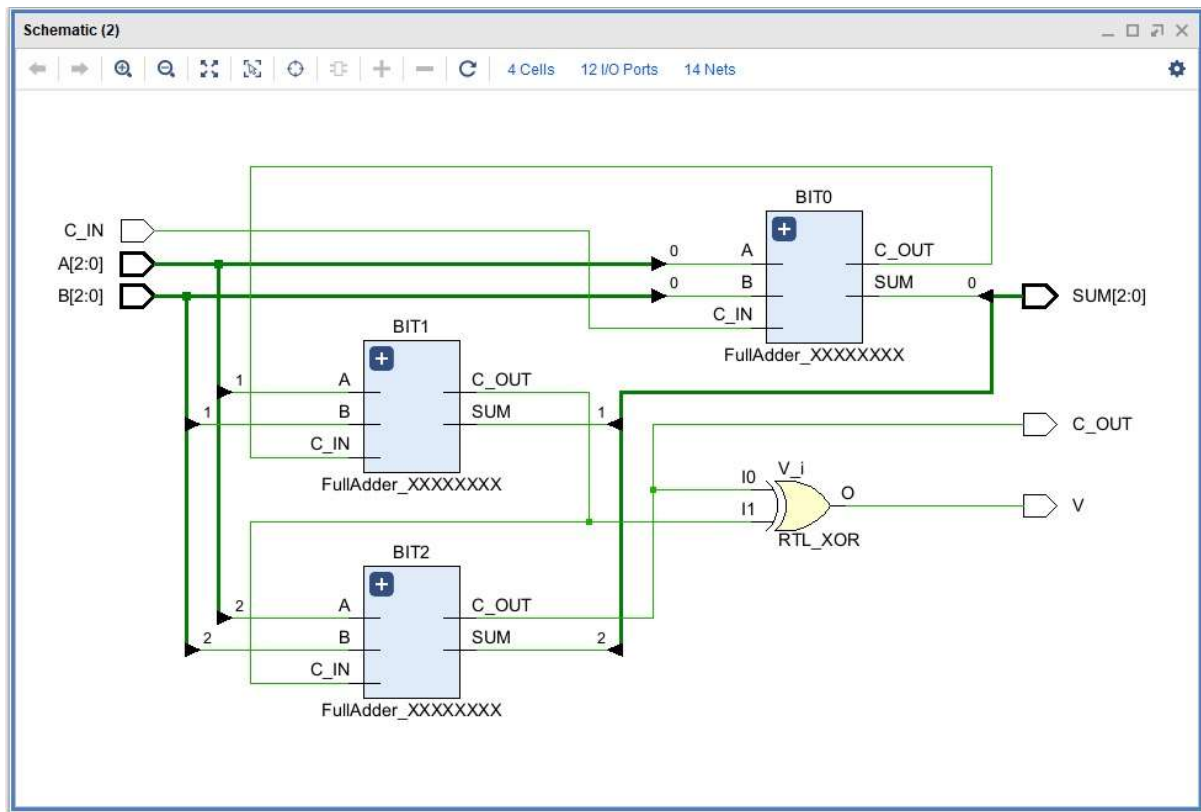
## RippleCarryAdder3Bit XXXXXXXX Schematic01.jpg



**You must take a screenshot of the schematic and save it in the JPG-file format.**
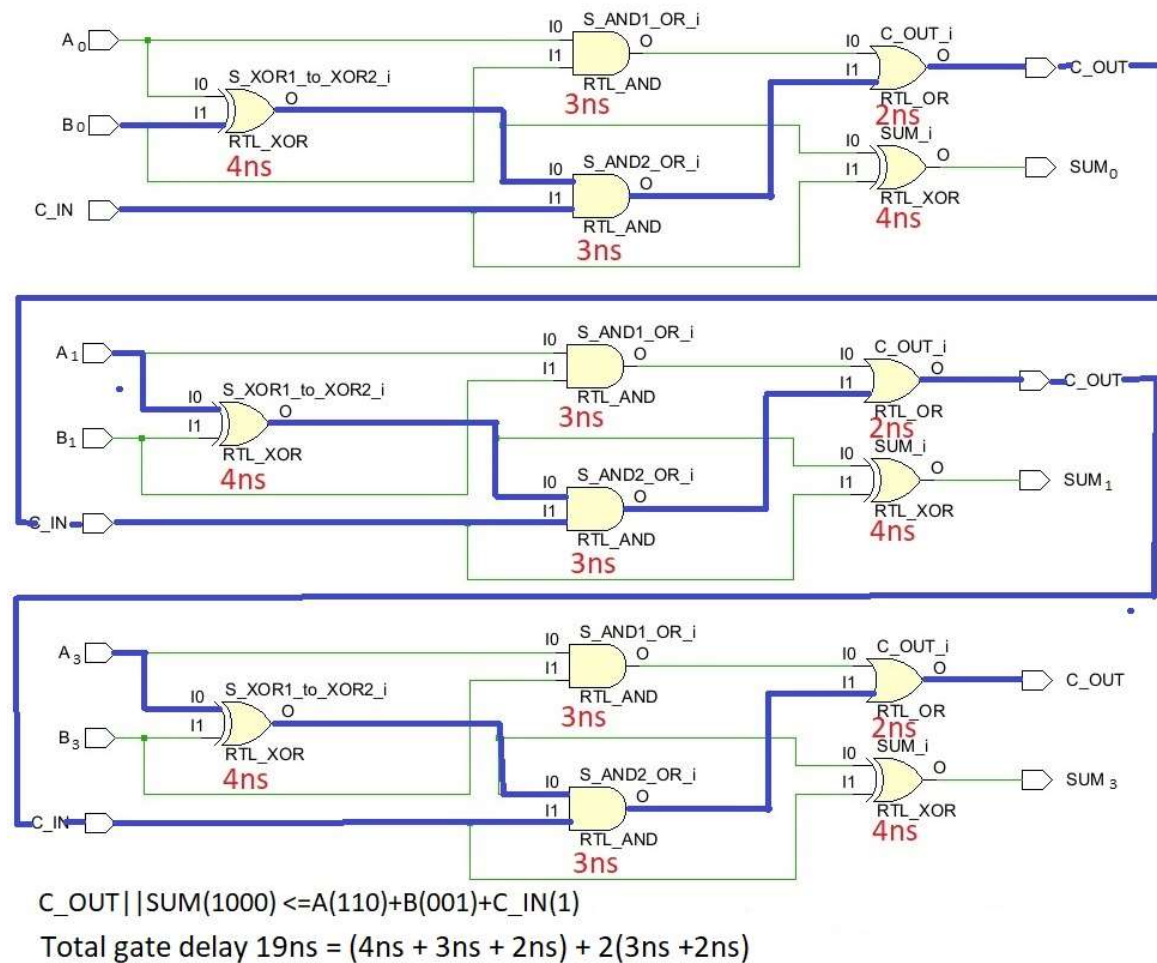
## RippleCarryAdder3Bit XXXXXXXX Schematic02.jpg



**You must take a screenshot of the schematic and save it in the JPG-file format.**

Furthermore, all entities must be tested according to the Simulation Procedure (CSU22022 Processor Project 2022-2023 Simulation Procedure V1.0).

**All files must be submitted to Blackboard as individual files, no zip-files.**

**You must print this checklist, tick the boxes, sign it, and submit it with your milestone assignment to Blackboard.**

**All files must be submitted in the checklist order:**

RF\_Mux16\_32Bit\_XXXXXXXX.vhd  
RF\_Mux16\_32Bit\_XXXXXXXX\_TB.vhd  
RF\_Mux16\_32Bit\_XXXXXXXX\_SchematicXX.jpg  
RF\_Mux16\_32Bit\_XXXXXXXX\_TDXX.jpg  
RF\_Mux16\_32Bit\_XXXXXXXX\_Doc.jpg  
RF\_Mux32\_32Bit\_XXXXXXXX.vhd  
RF\_Mux32\_32Bit\_XXXXXXXX\_TB.vhd  
RF\_Mux32\_32Bit\_XXXXXXXX\_SchematicXX.jpg  
RF\_Mux32\_32Bit\_XXXXXXXX\_TDXX.jpg  
RF\_Mux32\_32Bit\_XXXXXXXX\_Doc.jpg

- 
- 
- 

CSU22022 Processor Project 2022-2023 Checklist V1.0.pdf